

Problem:

Data = 8 bit

Address = 14 bit

Total Memory = 3 kbyte

Chip Size = 512 byte

Design a memory array.


Soln:

$$\begin{aligned}\text{Total chip} &= \frac{\text{Total Memory}}{\text{chip size}} = \frac{3K}{512} \\ &= \frac{3 \times 1024}{512} \\ &= 6\end{aligned}$$

$$512 = 2^9$$

$$A_{8-0} = 9$$

$$A_{7-0} = 8$$

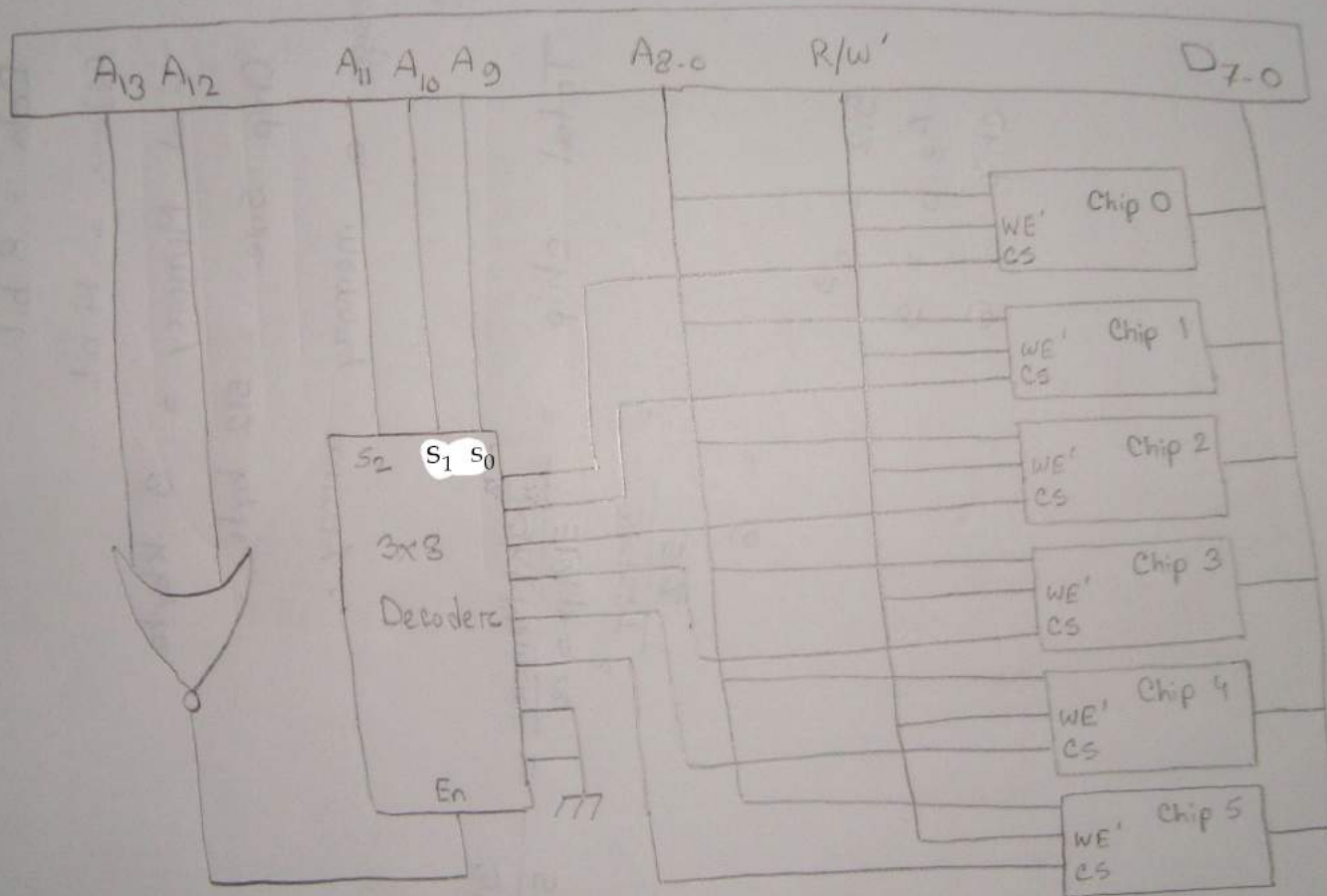

Problem :

Total Memory = 4 Kbyte

chip size = 1 kb

Data = 8 bit

Address Bit = 16


Design a memory array.

Soln:

$$\begin{aligned} \text{Total chip} &= \frac{\text{Total Memory}}{\text{chip size}} \\ &= \frac{4k}{1k} = 4 \end{aligned}$$

$$1024 = 2^{10}$$

$$A_{9-0} = 10$$

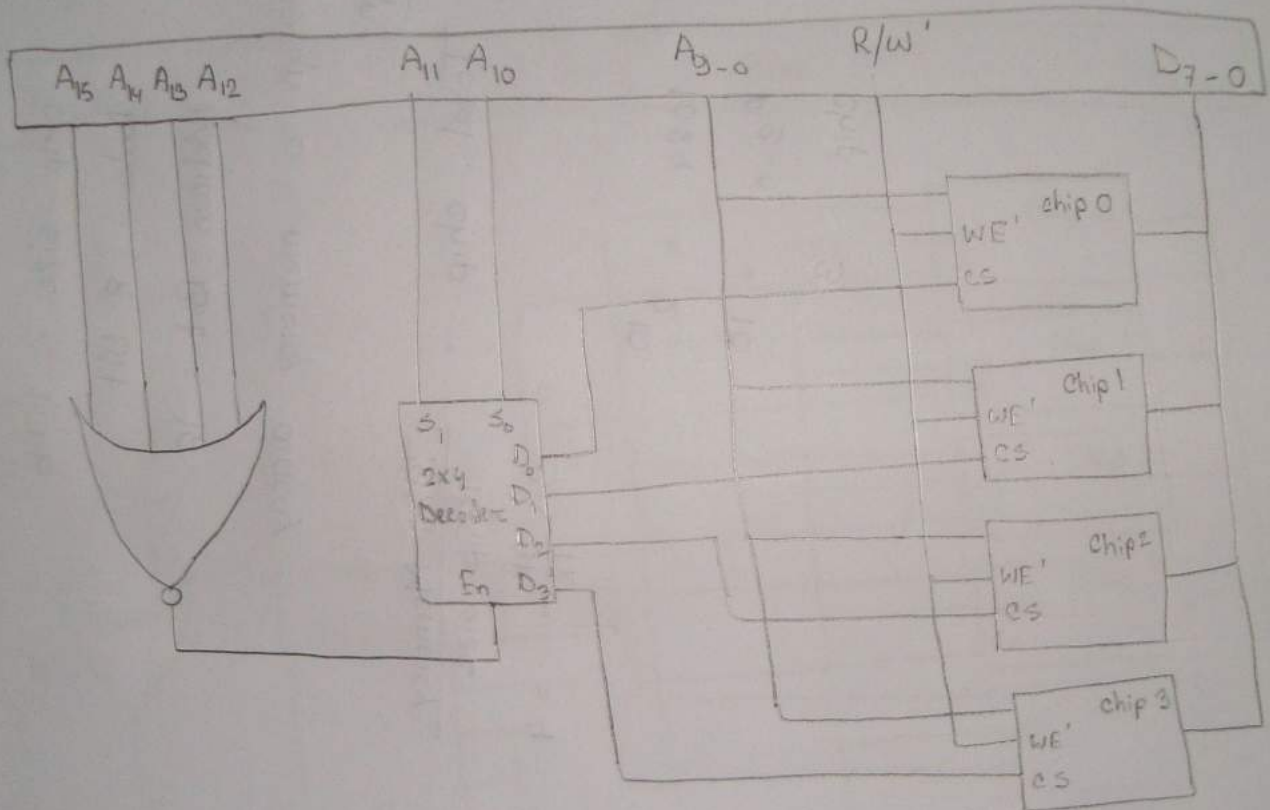

16 bits processor

Data Bus = 16 bits

Address Bus = 180 bits

chips = 7

size = 1M RAM

$$\begin{aligned}\therefore \text{Total Memory} &= 7 \times 1\text{M} \\ &= 7\text{M}\end{aligned}$$

$$1024 \times 1024 = 2^{20}$$

$$A_{19-0} = 20$$



# 16 bit Microprocessor

